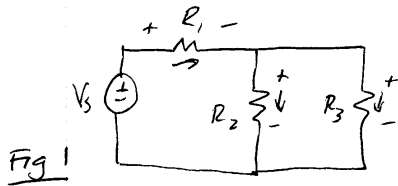



EE301/303 SPO9 HW2 SOLUTION

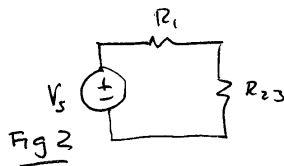PROBLEM 1




Given: $V_s = 30V$, $R_1 = R_2 = R_3 = 500\Omega$
 Find: i_{R1}
 i_{R2}
 i_{R3}
 V_{R1} , V_{R2} , V_{R3}

$$R_{23} = R_2 \parallel R_3 = \frac{1}{\frac{1}{500} + \frac{1}{500}} = 250\Omega$$



$$R_{eq} = R_{123} = R_1 + R_{23} = 500 + 250 = \underline{\underline{750\Omega = R_{eq}}}$$
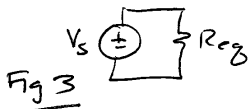
$$i_{V_s} = \frac{V_s}{R_{eq}} = \frac{30}{750}$$



$$\underline{\underline{i_{V_s} = 0.04A = 40mA \leftarrow}}$$

Using Fig 2: $V_{R1} = \frac{R_1}{R_1 + R_{23}} \cdot V_s = \frac{500}{500 + 250} \cdot 30$

$$\underline{\underline{V_{R1} = 20V \leftarrow}}$$

$$V_{R23} = \frac{R_{23}}{R_1 + R_{23}} \cdot V_s = \frac{250}{500 + 250} \cdot 30$$

$$V_{R23} = 10V$$

$$i_{R1} = i_{R23} = i_{V_s}$$

$$\underline{\underline{i_{R1} = 40mA \leftarrow}}$$

Using Fig 3: $V_{R2} = V_{R3} = V_{R23} = 10V \rightarrow \underline{\underline{V_{R2} = 10V \leftarrow}}$

$$\underline{\underline{V_{R3} = 10V \leftarrow}}$$

$$i_{R2} = \frac{\frac{1}{R_2}}{\frac{1}{R_2} + \frac{1}{R_3}} \cdot i_{R1} = \frac{R_3}{R_2 + R_3} \cdot i_{R1}$$

$$= \frac{500}{500 + 500} \cdot 40mA$$

$$\underline{\underline{i_{R2} = 20mA}}$$

$$i_{R3} = \frac{\frac{1}{R_3}}{\frac{1}{R_2} + \frac{1}{R_3}} \cdot i_{R1} = \frac{R_2}{R_2 + R_3} \cdot i_{R1}$$

$$= \frac{500}{500 + 500} \cdot 40mA$$

$$\underline{\underline{i_{R3} = 20mA \leftarrow}}$$

PROBLEM 2

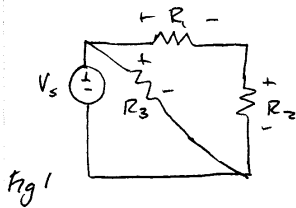


Fig 1

$$R_1 + R_2 = R_{12} = 100 + 200$$

$$R_{12} = 300$$

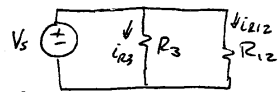


Fig 2

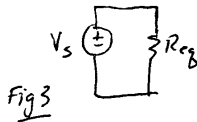


Fig 3

GIVEN: $V_s = 30V$, $R_1 = 100\Omega$
 $R_2 = 200\Omega$, $R_3 = 300\Omega$

FIND: R_{eq}
 i_{V_s}
 i_{R_1} , i_{R_2} , i_{R_3}
 V_{R_1} , V_{R_2} , V_{R_3}

$$R_{123} = R_{eq} = R_{12} \parallel R_3 = \frac{1}{\frac{1}{300} + \frac{1}{300}} = 150\Omega$$

$$i_{V_s} = \frac{V_s}{R_{eq}} = \frac{30}{150} = 0.2A = 200mA = i_{V_s}$$

From Fig 2 $V_s = V_{R_3} = 30V \leftarrow$

$$V_{R_{12}} = V_s = 30V$$

$$i_{R_3} = \frac{\frac{1}{R_3}}{\frac{1}{R_3} + \frac{1}{R_{12}}} \cdot i_{V_s} = \frac{\frac{1}{300}}{\frac{1}{300} + \frac{1}{300}} \cdot 200mA = 100mA = i_{R_3} \leftarrow$$

$$i_{R_{12}} = \frac{\frac{1}{R_{12}}}{\frac{1}{R_3} + \frac{1}{R_{12}}} \cdot i_{V_s} = \frac{\frac{1}{300}}{\frac{1}{300} + \frac{1}{300}} \cdot 200mA = 100mA = i_{R_{12}}$$

From Fig 1

$$i_{R_1} = i_{R_2} = i_{R_{12}} \Rightarrow i_{R_1} = 100mA \leftarrow$$

$$i_{R_2} = 100mA \leftarrow$$

$$V_{R_1} = \frac{R_1}{R_1 + R_2} \cdot V_{R_{12}} = \frac{100}{100 + 200} \cdot 30 = 10V = V_{R_1} \leftarrow$$

$$V_{R_2} = \frac{R_2}{R_1 + R_2} \cdot V_{R_{12}} = \frac{200}{100 + 200} \cdot 30 = 20V = V_{R_2} \leftarrow$$

PROBLEM 3

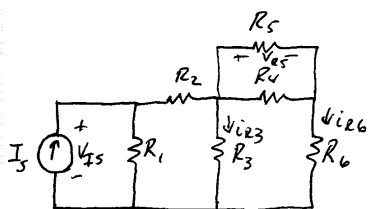


Fig 1

$$R_{45} = R_4 \parallel R_5 = \frac{1}{\frac{1}{20} + \frac{1}{20}} = 10 \Omega$$

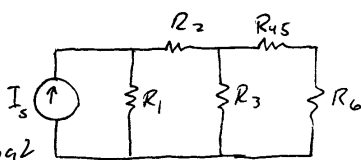


Fig 2

$$R_{36} = R_3 \parallel R_6 = 30 \parallel 10 = 7.5 \Omega$$

$$R_{456} = R_6 + R_{36} = 10 + 7.5 = 17.5 \Omega$$

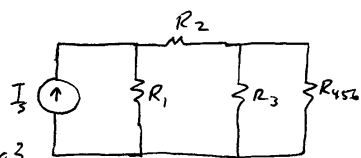


Fig 3

$$R_{3456} = R_3 \parallel R_{456} = \frac{1}{\frac{1}{20} + \frac{1}{17.5}} = 13 \frac{1}{3} \Omega$$

$$R_{3456} = 13 \frac{1}{3} \Omega$$

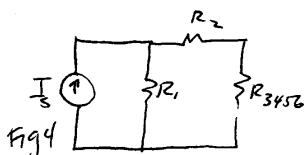


Fig 4

$$R_{236} = R_2 + R_{3456} = 10 + 13 \frac{1}{3} = 23 \frac{1}{3} \Omega$$

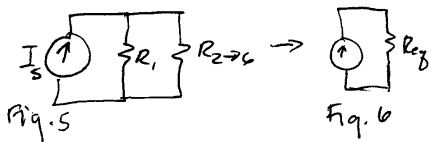


Fig 5

Fig 6

GIVEN: $R_1 = 20 \Omega$, $R_2 = 10 \Omega$
 $R_3 = R_4 = R_5 = 20 \Omega$
 $R_6 = 30 \Omega$
 $I_s = 5A$

FIND: R_{eq}

- i_{R3}, i_{R6}
- V_{R5}, V_{I5}

From Fig 6 $V_{I5} = I_s R_{eq}$
 $= 5(10.77)$

$$V_{I5} = 53.85V \leftarrow$$

From Fig 5: $V_{R1} = V_{R236} = V_{I5} = 53.85V$

$$i_{R236} = \frac{V_{R236}}{R_{236}} = \frac{53.85}{23.3} = 2.31A$$

$$i_{R236} = 2.31A$$

From Fig 4: $i_{R2} = i_{R36} = i_{R236} = 2.31A$

$$V_{R3456} = \frac{R_{3456}}{R_2 + R_{3456}} \cdot V_{R236}$$

$$= \frac{13.3}{10 + 13.3} \cdot 53.85$$

$$V_{R3456} = 30.77V$$

CONT. ON NEXT PAGE.

$$R_{eq} = R_1 \parallel R_{236} = \frac{1}{\frac{1}{20} + \frac{1}{23 \frac{1}{3}}} = 10.77 \Omega = R_{eq}$$

PROBLEM 3 CONT.

FROM FIG. 3

$$V_{R3} = V_{R456} = V_{R3456} = 30.77 \text{ V}$$

$$i_{R3} = \frac{\frac{1}{R_3}}{\frac{1}{R_3} + \frac{1}{R_{456}}} \cdot i_{R3 \rightarrow 6}$$

$$= \frac{\frac{1}{20}}{\frac{1}{20} + \frac{1}{40}} \cdot 2.31$$

$$\underline{i_{R3} = 1.54 \text{ A} \leftarrow}$$

$$i_{R456} = \frac{\frac{1}{R_{456}}}{\frac{1}{R_3} + \frac{1}{R_{456}}} \cdot i_{R3 \rightarrow 6}$$

$$= \frac{\frac{1}{40}}{\frac{1}{20} + \frac{1}{40}} \cdot 2.31$$

$$i_{R456} = 0.77 \text{ A}$$

FROM FIG. 2 $i_{R45} = i_{R6} = i_{R456}$

$$\underline{i_{R6} = 0.77 \text{ A} \leftarrow}$$

$$V_{R45} = \frac{R_{45}}{R_{45} + R_6} \cdot V_{R456}$$


$$= \frac{10}{10 + 30} \cdot 30.77$$

$$V_{R45} = 7.69 \text{ V}$$

FROM FIG. 1 $V_{R4} = V_{R5} = V_{R45}$

$$\underline{V_{R5} = 7.69 \text{ V} \leftarrow}$$

PROBLEM 4

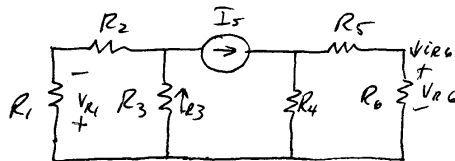


GIVEN: $R_1 = 15\Omega$, $R_2 = 15\Omega$
 $R_3 = 30\Omega$, $R_4 = 40\Omega$
 $R_5 = 20\Omega$, $R_6 = 20\Omega$
 $I_s = 100\text{ mA}$

FIND i_{R3} , i_{R6} , V_{R1} , V_{R4}

$$R_{12} = R_1 + R_2 = 15 + 15 = 30\Omega$$

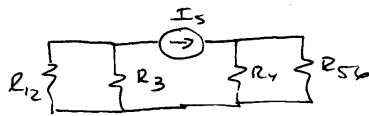
$$R_{56} = R_5 + R_6 = 20 + 20 = 40\Omega$$






$$R_{123} = R_{12} \parallel R_3 = \frac{1}{\frac{1}{R_{12}} + \frac{1}{R_3}} = \frac{1}{\frac{1}{30} + \frac{1}{30}}$$

$$R_{123} = 15\Omega$$
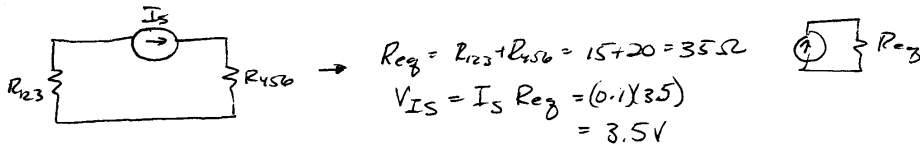
$$R_{456} = R_4 \parallel R_{56} = \frac{1}{\frac{1}{40} + \frac{1}{40}} = 20\Omega$$



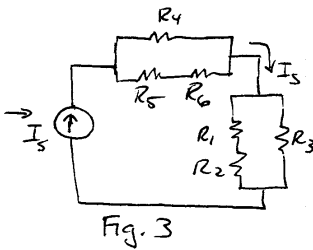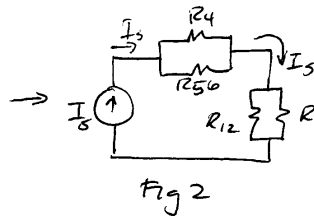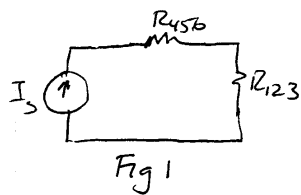THIS PROBLEM IS EASIER TO SOLVE IF WE REDRAW.



FROM FIG. 1

$$I_s = i_{R_{456}} = i_{R_{123}}$$

$$V_{R_{456}} = \frac{R_{456}}{R_{456} + R_{123}} \cdot V_{IS}$$

$$= \frac{20}{20 + 15} \cdot 3.5$$

$$V_{R_{456}} = 2\text{ V}$$

$$V_{R_{123}} = \frac{R_{123}}{R_{456} + R_{123}} \cdot V_{IS}$$

$$= \frac{15}{20 + 15} \cdot 3.5$$

$$V_{R_{123}} = 1.5\text{ V}$$

PROBLEM 4 CONT.

$$\text{FROM FIG 2: } V_{R4} = V_{R56} = V_{R456} = 2V$$

$$V_{R12} = V_{R3} = V_{R123} = 1.5V$$

$$i_{R56} = \frac{\frac{1}{R_{56}}}{\frac{1}{R_4} + \frac{1}{R_{56}}} \cdot I_S = \frac{\frac{1}{40}}{\frac{1}{40} + \frac{1}{40}} = 100mA = 50mA = i_{R56}$$

$$i_{R3} = \frac{\frac{1}{R_3}}{\frac{1}{R_3} + \frac{1}{R_{12}}} \cdot I_S = \frac{\frac{1}{30}}{\frac{1}{30} + \frac{1}{30}} \cdot 100 = \underline{\underline{50mA = i_{R3}}} \leftarrow$$

FROM FIG 3:

$$i_{R5} = i_{R6} = i_{R56}$$


$$\underline{\underline{i_{R6} = 50mA}} \leftarrow$$

$$V_{R6} = \frac{R_6}{R_5 + R_6} \cdot V_{R56} = \frac{20}{20+20} \cdot 2 \Rightarrow \underline{\underline{V_{R6} = 1V}}$$

$$V_{R1} = \frac{R_1}{R_1 + R_2} \cdot V_{R12} = \frac{15}{15+15} \cdot 1.5 \Rightarrow \underline{\underline{V_{R1} = 0.75V}} \leftarrow$$

EE301/303 SP07 HW2 SOLUTION

PROBLEMS

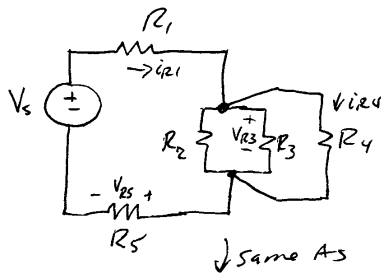

GIVEN: $R_1 = 15\Omega$, $R_2 = 10\Omega$,
 $R_3 = 5\Omega$, $R_4 = 10\Omega$
 $R_5 = 2.5\Omega$, $V_s = 5V$

FIND: i_{R1} , i_{R4} , V_{R3} , V_{R5}
 R_{eq}

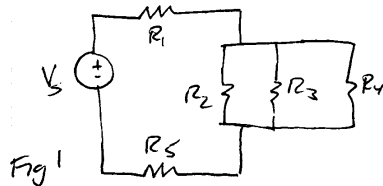


Fig 1

$$R_{234} = R_2 // R_3 // R_4$$

$$= \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = \frac{1}{\frac{1}{10} + \frac{1}{5} + \frac{1}{10}} = 2.5\Omega$$

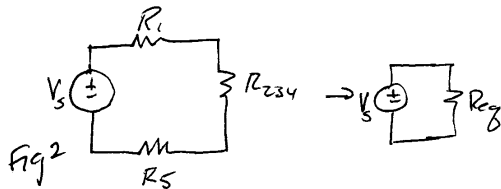


Fig 2

$$R_{1 \rightarrow 5} = R_1 + R_{234} + R_5$$

$$= 15 + 2.5 + 2.5 = 20\Omega$$

$$R_{eq} = 20\Omega \leftarrow$$

$$i_{V_s} = \frac{V_s}{R_{eq}} = \frac{5}{20}$$

$$i_{V_s} = 0.25A$$

FROM Fig. 2

$$i_{R1} = i_{R234} = i_{R5} = i_{V_s}$$

$$i_{R1} = 0.25A \leftarrow$$

$$V_{R234} = \frac{R_{234}}{R_1 + R_{234} + R_5} \cdot V_s$$

$$= \frac{2.5}{15 + 2.5 + 2.5} \cdot 5$$

$$V_{R234} = 0.625V$$

$$V_{R5} = \frac{R_5}{R_1 + R_{234} + R_5} \cdot V_s$$

$$= \frac{2.5}{15 + 2.5 + 2.5} \cdot 5 = 0.625$$

$$V_{R5} = 0.625V \leftarrow$$

FROM Fig. 1

$$V_{R3} = V_{R234} = 0.625V$$

$$V_{R3} = 0.625V \leftarrow$$

$$i_{R4} = \frac{1}{R_4} \cdot i_{V_s}$$


$$\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$= \frac{1}{10} \cdot 0.25$$

$$\frac{1}{10} + \frac{1}{5} + \frac{1}{10}$$

$$i_{R4} = 0.0625A \leftarrow$$

PROBLEM 6

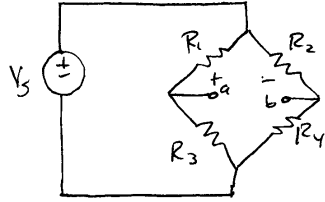

GIVEN: $V_s = 6V$, $R_1 = 5\Omega$, $R_2 = 10\Omega$
 $R_3 = 10\Omega$, $R_4 = 5\Omega$

FIND: THE VOLTAGE BETWEEN
NODES a & b V_{ab}


$$V_a = V_{R_3} = \frac{R_3}{R_1 + R_3} \cdot V_s$$
$$= \frac{10}{5 + 10} \cdot 6 = 4V$$

$$V_b = V_{R_4} = \frac{R_4}{R_2 + R_4} \cdot V_s$$
$$= \frac{5}{5 + 10} \cdot 6 = 2V$$

$$V_{ab} = V_a - V_b = 4 - 2 = \underline{\underline{2V = V_{ab}}} \leftarrow$$

EE301/303 SP09 HW 2 SOLUTION

PROBLEM 7

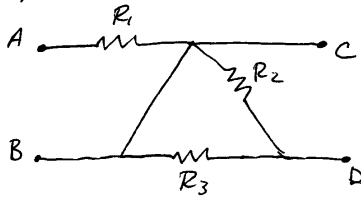


GIVEN: $R_1 = 60\Omega$ $R_2 = 100\Omega$
 $R_3 = 100\Omega$

FIND: $R_{AB}, R_{BC}, R_{AC}, R_{CD}$
 R_{BD}, R_{AD}

R_{AB}


(NOTICE NODES C & B ARE THE SAME)

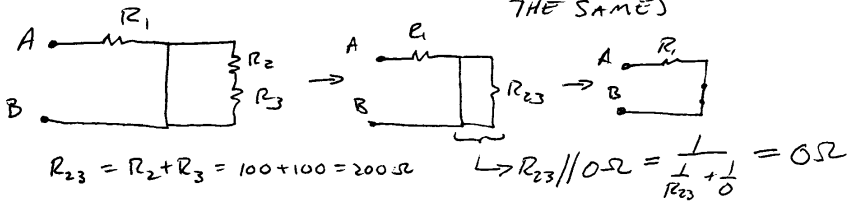


$R_{AB} = R_1 = 60\Omega = R_{AB} \leftarrow$

RESISTOR IS DIRECTLY SHORTED


R_{BC}

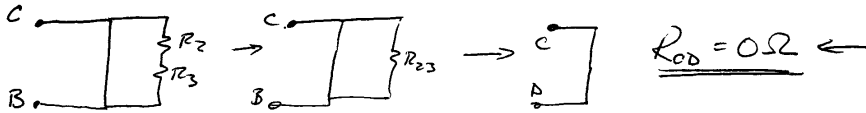

R_{AC}

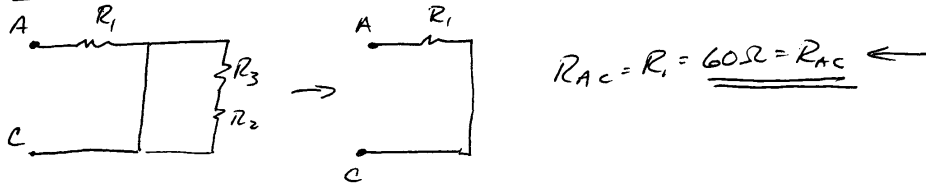


R_{CD}


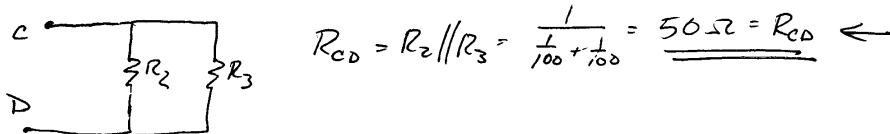


PROBLEM 7 CONT.

R_{BD}

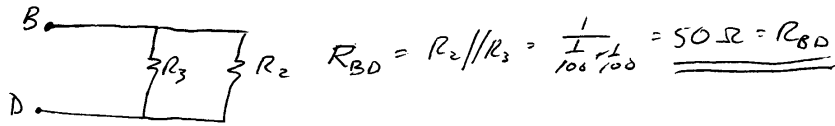

R_{AD}

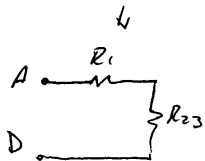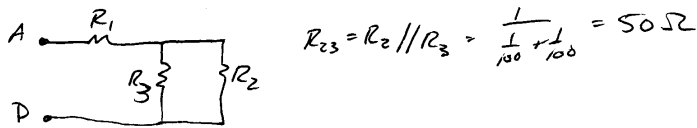


$$R_{AD} = R_1 + R_{23} = 60 + 50$$

$$\underline{R_{AD} = 110 \Omega} \leftarrow$$

EES01/303 SP08 HW #2 SOLUTION

PROBLEM 2.47

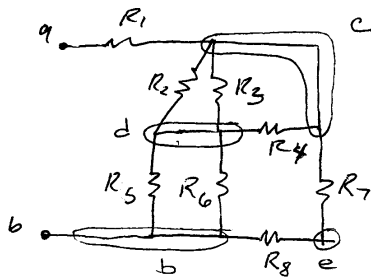

GIVEN $R_1 = 3\Omega$, $R_2 = 6\Omega$, $R_3 = 12\Omega$
 $R_4 = 4\Omega$, $R_5 = 4\Omega$, $R_6 = 4\Omega$
 $R_7 = 2\Omega$, $R_8 = 2\Omega$

FIND: R_{ab}

R_2, R_3 & R_4 SHARE THE SAME 2 TERMINALS SO THEY ARE IN PARALLEL

$$R_{234} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = \frac{1}{\frac{1}{6} + \frac{1}{12} + \frac{1}{4}}$$

$$R_{234} = 2\Omega \quad \leftarrow \text{(Between c \& d)}$$

R_5 & R_6 ARE IN PARALLEL

$$R_{56} = \frac{1}{\frac{1}{R_5} + \frac{1}{R_6}} = \frac{1}{\frac{1}{4} + \frac{1}{4}} = 2\Omega \quad \leftarrow$$

between d & b

R_7 & R_8 ARE IN SERIES

$$R_{78} = R_7 + R_8 = 2 + 2$$


$$R_{78} = 4\Omega \quad \leftarrow$$

between c & b

$$R_{23456} = R_{234} + R_{56}$$


$$= 2 + 2$$

$$R_{2 \rightarrow 6} = 4\Omega$$

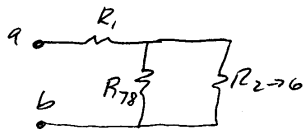

$$R_{2 \rightarrow 8} = R_{78} \parallel R_{2 \rightarrow 6} = \frac{1}{\frac{1}{4} + \frac{1}{4}} =$$

$$R_{2 \rightarrow 8} = 2\Omega$$

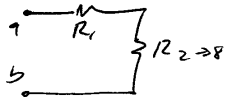


$$R_{ab} = R_1 + R_{2 \rightarrow 8}$$

$$= 3 + 2$$

$$\underline{\underline{R_{ab} = 5\Omega \quad \leftarrow}}$$

EE301/303 SP08 HW#2 SOLUTION

PROBLEM 2.59

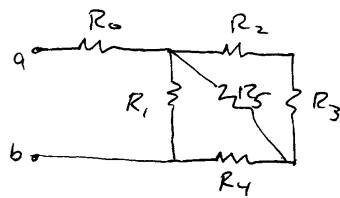

GIVEN: $R_0 = 4\Omega$, $R_1 = 12\Omega$, $R_2 = 8\Omega$
 $R_3 = 2\Omega$, $R_4 = 16\Omega$, $R_5 = 5\Omega$


FIND: R_{ab}

$$R_{23} = R_2 + R_3 = 8 + 2 = 10\Omega = R_{23}$$




$$R_{235} = R_{23} \parallel R_4 = \frac{1}{\frac{1}{R_{23}} + \frac{1}{R_4}}$$
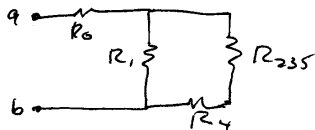
$$= \frac{1}{\frac{1}{10} + \frac{1}{5}} = 3\frac{1}{3}\Omega$$




$$R_{2345} = R_4 + R_{235} = 16 + 3\frac{1}{3}$$

$$R_{2345} = 19\frac{1}{3}\Omega$$

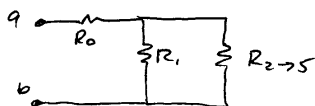

$$R_{12345} = R_1 \parallel R_{2345} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_{2345}}}$$

$$R_{12345} = 7.4\Omega$$

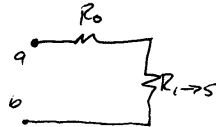


$$R_{ab} = R_0 + R_{12345}$$

$$= 4 + 7.4$$

$$\underline{\underline{R_{ab} = 11.4\Omega}}$$

EE301/303 SP08 HW#2 SOLUTION

PROBLEM 2.64

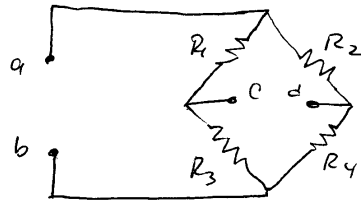


Given: $R_1 = 360\Omega$, $R_2 = 180\Omega$
 $R_3 = 540\Omega$, $R_4 = 540\Omega$

FIND: R_{ab} if 1) cd OPEN
 2) cd SHORTED


R_{cd} if 1) ab OPEN
 2) ab SHORTED

R_{ab} w/ cd OPEN

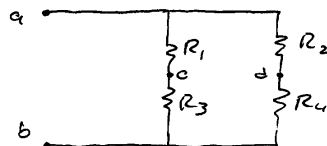

$$R_{13} = R_1 + R_3 = 360 + 540 = 900\Omega = R_{13}$$


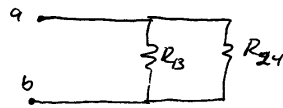
$$R_{24} = R_2 + R_4 = 180 + 540 = 720\Omega = R_{24}$$



$$R_{ab} = R_{13} \parallel R_{24} = \frac{1}{\frac{1}{R_{13}} + \frac{1}{R_{24}}} = \frac{1}{\frac{1}{900} + \frac{1}{720}}$$

$$\underline{R_{ab} = 400\Omega} \leftarrow$$

R_{ab} w/ cd SHORTED

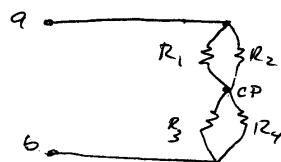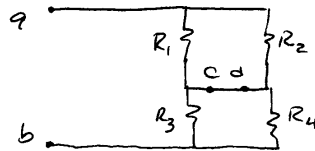

$$R_{12} = R_1 \parallel R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{\frac{1}{360} + \frac{1}{180}} = 120\Omega = R_{12}$$


$$R_{34} = R_3 \parallel R_4 = \frac{1}{\frac{1}{R_3} + \frac{1}{R_4}} = \frac{1}{\frac{1}{540} + \frac{1}{540}} = 270\Omega = R_{34}$$

$$R_{ab} = R_{12} + R_{34} = 120 + 270 = 390\Omega$$

$$\underline{R_{ab} = 390\Omega} \leftarrow$$


PROBLEM 2.64 CONT.

R_{cd} w/ab OPEN

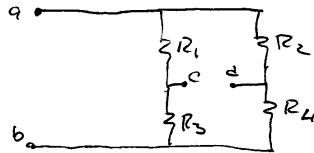


$$R_{12} = R_1 + R_2 = 360 + 180 = 540 \Omega = R_{12}$$
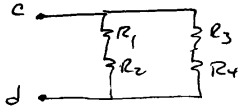
$$R_{34} = R_3 + R_4 = 540 + 540 = 1080 \Omega = R_{34}$$




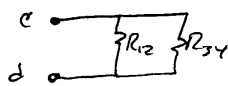
$$R_{cd} = R_{12} \parallel R_{34} = \frac{1}{\frac{1}{R_{12}} + \frac{1}{R_{34}}} = \frac{1}{\frac{1}{540} + \frac{1}{1080}} = 360$$



$R_{cd} = 360 \Omega$ ←

R_{cd} w/ab shorted

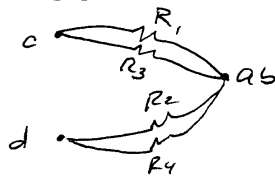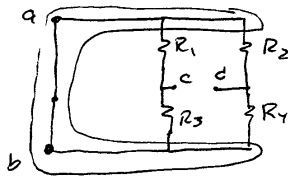


$$R_{13} = R_1 \parallel R_3 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_3}} = \frac{1}{\frac{1}{360} + \frac{1}{540}} = 216 \Omega = R_{13}$$


$$R_{24} = R_2 \parallel R_4 = \frac{1}{\frac{1}{R_2} + \frac{1}{R_4}} = \frac{1}{\frac{1}{180} + \frac{1}{540}} = 135 \Omega = R_{24}$$

$$R_{cd} = R_{13} + R_{24} = 216 + 135$$

$R_{cd} = 351 \Omega$ ←

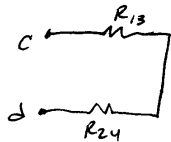

PROBLEM 279

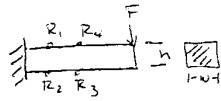

Given $V_{BA} = 50 \text{ mV}$

Find F when $R_0 = 1 \text{ k}\Omega$


$w = 25 \text{ mm}$

$V_s = 12 \text{ V}$

$h = 100 \text{ mm}$

$L = 0.3 \text{ m}$

$\gamma = 69 \text{ GN/m}^2$

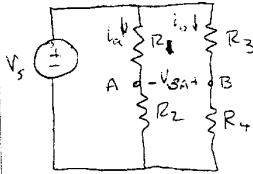

$$R_1 = R_4 = R_0 + \Delta R$$

$$R_2 = R_3 = R_0 - \Delta R$$

$$i_A = \frac{V_s}{R_1 + R_2} \quad i_B = \frac{V_s}{R_3 + R_4}$$

$$V_A = \frac{R_2}{R_1 + R_2} \cdot V_s \quad V_B = \frac{R_4}{R_3 + R_4} \cdot V_s$$

$$V_{BA} = V_B - V_A = \frac{R_4}{R_3 + R_4} \cdot V_s - \frac{R_2}{R_1 + R_2} \cdot V_s$$

$$V_{BA} = V_s \left(\frac{R_4}{R_3 + R_4} - \frac{R_2}{R_1 + R_2} \right)$$

$$V_s \left(\frac{R_0 + \Delta R}{R_0 - \Delta R + R_0 + \Delta R} - \frac{R_0 - \Delta R}{R_0 + \Delta R + R_0 - \Delta R} \right)$$

$$V_{BA} = V_s \cdot \frac{2\Delta R}{2R_0} = \frac{\Delta R}{R_0} V_s$$

$$\Delta R = R_0 \epsilon F \quad F \text{ is gauge factor } F_0 = 2$$

$$\Delta R = \frac{R_0 \epsilon L F F_0}{w h^2 \gamma} \Rightarrow V_{BA} = \frac{R_0 \epsilon L F F_0 V_s}{w h^2 \gamma R_0}$$

$$F = \frac{V_{BA} w h^2 \gamma}{\epsilon F_0 V_s} = \frac{(50 \times 10^{-3}) (25 \times 10^{-3}) (100 \times 10^{-3})^2 (69 \times 10^9)}{6 (0.3) (12) (2)}$$

$$F = 19.96 \text{ kN} \leftarrow$$

22-141 63 SHEETS
22-142 60 SHEETS
22-143 60 SHEETS
22-144 200 SHEETS